


Shifter schematic. by using 4x 1-bit shifter.

Op[15:0]

Cnt[3:0]

In[15:0]

Top-level design.

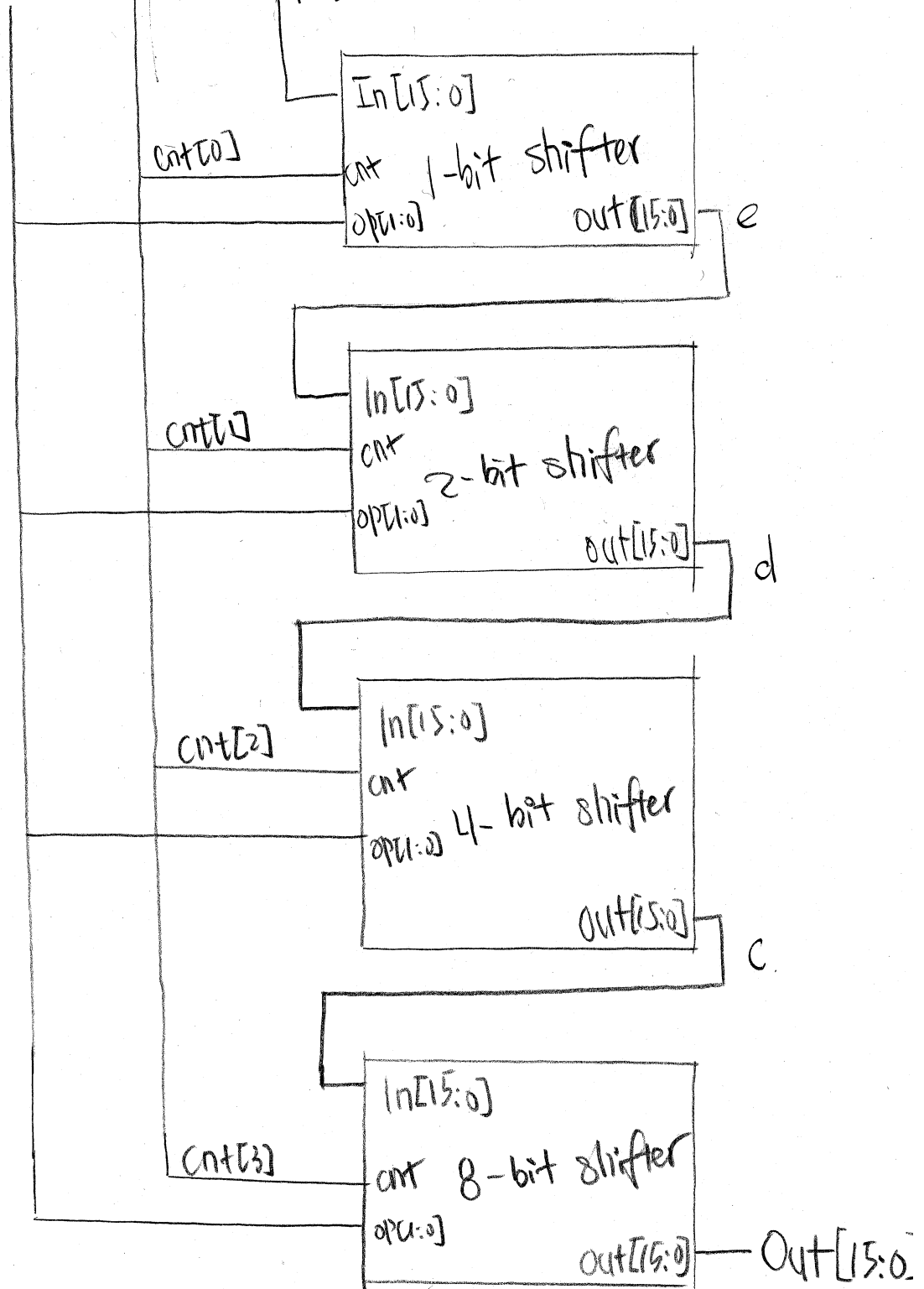

Reference to Prof Sathi 657 - 2011

Opcode Generator - 1. Opcode generator 0, 2, 3 can be empty.

